

DATE:

VERIFICATION OF NORTON'S THEOREM

EXP-05

AIM:

To verify Norton's theorem practically and theoretically for the given DC circuit.

APPARATUS REQUIRED:


SNO	APPARATUS	SPECIFICATION	QUANTITY
1	Regulated power supply	(0-30)V	1
2	Voltmeter	(0-30)V	1
3	Ammeter	(0-10mA) MC	1
4	Resistor	470 Ω , 560 Ω , 1K Ω	2, 1, 1
5	Bread board		1
6	Multimeter		1

PROCEDURE:


1. Mark the connections as per the circuit diagram 1.
2. Vary the RPS and set an input voltage of 10V
3. Note down the voltmeter reading (V_i) and ammeter reading (I_i) in the tabular column 1.
4. Switch off the supply and make connections for the circuit diagram
5. Measure the Thevenin's resistance
 $R_{Th} = \text{Norton's Resistance } R_N$
6. Switch off the supply of 10V in the RPS and note down the voltmeter reading V_i and V_{Th}

CIRCUIT DIAGRAM: VERIFICATION OF NORTON'S THEOREM


To measure I_L :

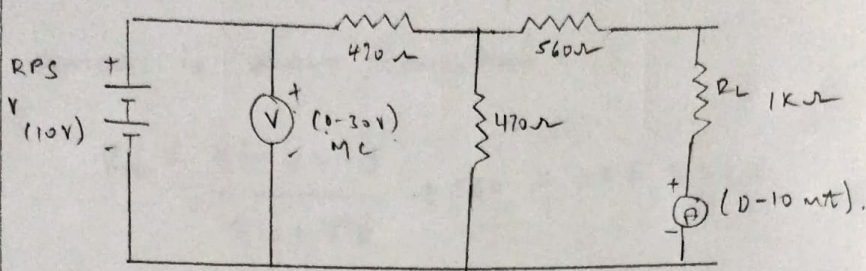


To measure R_{th} or R_N

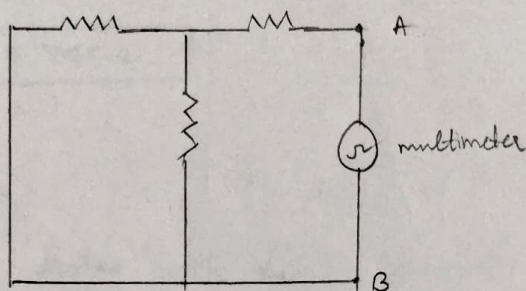


To measure I_N or I_{sc} :

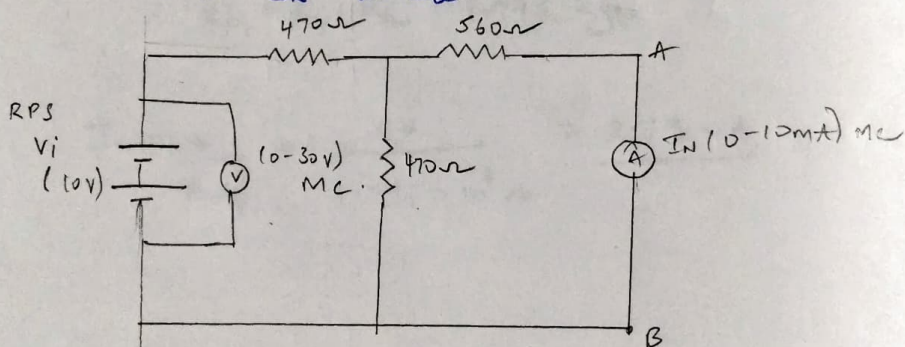

Theremin's equivalent criteria:

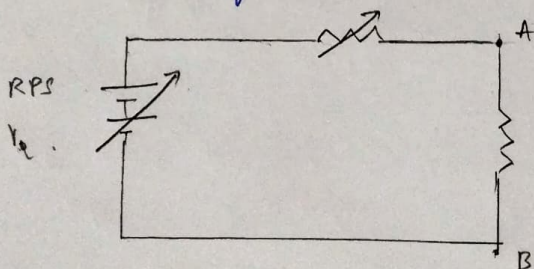

Norton's equivalent criteria:

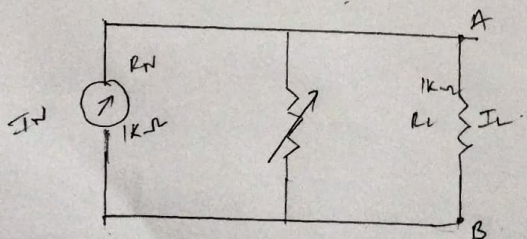

Tabular column 1:

To measure I_L :

V_i (volt)	I_L (amps)
10	2.86 A

in tabular column 3.

7. Set an input voltage of 10V in the RPS and note down the voltmeter reading V_i and $V_{th} = V_{oc}$.

8. Switch off the supply and make connections for the circuit diagram 4.

9. Set an input voltage of 10V in the RPS and note down the voltmeter V_i and the ammeter reading I_N [sc] in tabular column 4.

10. Draw the Thevenin's equivalent circuit and Norton's equivalent circuit as shown in a circuit diagrams 5 and 6 respectively.

11. Calculate the I_L value using the formula
Thevenin's theorem

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

Norton's Theorem

$$I_L = \frac{I_N \times R_N}{R_N + R_L}$$

12. Theoretically verify the Norton's theorem

$$V_L = \frac{0.02 \times 0.1}{(0.02) + 0.1} = \frac{0.002}{0.12} = 0.0167 \text{ V}$$

RESULT

Thus Thevenin's and Norton's theorem is verified practically and theoretically.

TABULAR COLUMN 2:

To measure R_{th} or R_N

V_i (Volt)	R_{th} (Ω)
10 V	773 Ω

TABULAR COLUMN 3:

To measure I_N or I_{sc}

V_i (volt)	I_N (milliamp)
10	6.38 mA

MODEL CALCULATION:

Practical value of I_L (from tabulation 1) = 2.3 mA
 verification of Norton's theorem

$$I_L = \frac{I_N \times R_N}{R_N + R_L} = 2.43 \text{ mA}$$

Theoretical calculation of I_L , I_N and R_{th} (R_N) for the given circuit.

THEORETICAL CALCULATION:

Parallel R_3 and R_2 after short circuit, R_L .

$$R_{par} = \frac{560 \times 470}{560 + 470} = 255.53 \Omega$$

at node A,

$$V_A = \frac{10V \times R_{par}}{R_1 + R_{par}} = \frac{10 \times 255.53}{470 + 255.53}$$

$$V_A = 3.52V$$

Current Through 560Ω ,

$$I_{sc} = \frac{V_A}{560} = \frac{3.52}{560} = 6.285 \text{ mA}$$

$$R_N = \frac{470 \times 470}{470 + 470} + 560 = 795 \Omega \quad \therefore R_N = 795 \Omega$$

$$\therefore I_L = \frac{I_N \times R_N}{R_N + R_L} = \frac{6.285 \text{ mA} \times 795}{795 + 1000}$$

$$I_L = 2.79 \text{ mA}$$